


# An Introduction to VLSI (Very Large Scale Integrated) Circuit Design

---


*Presented at EE1001  
Oct. 16th, 2018*

By Hua Tang

# *The first electronic computer (1946)*

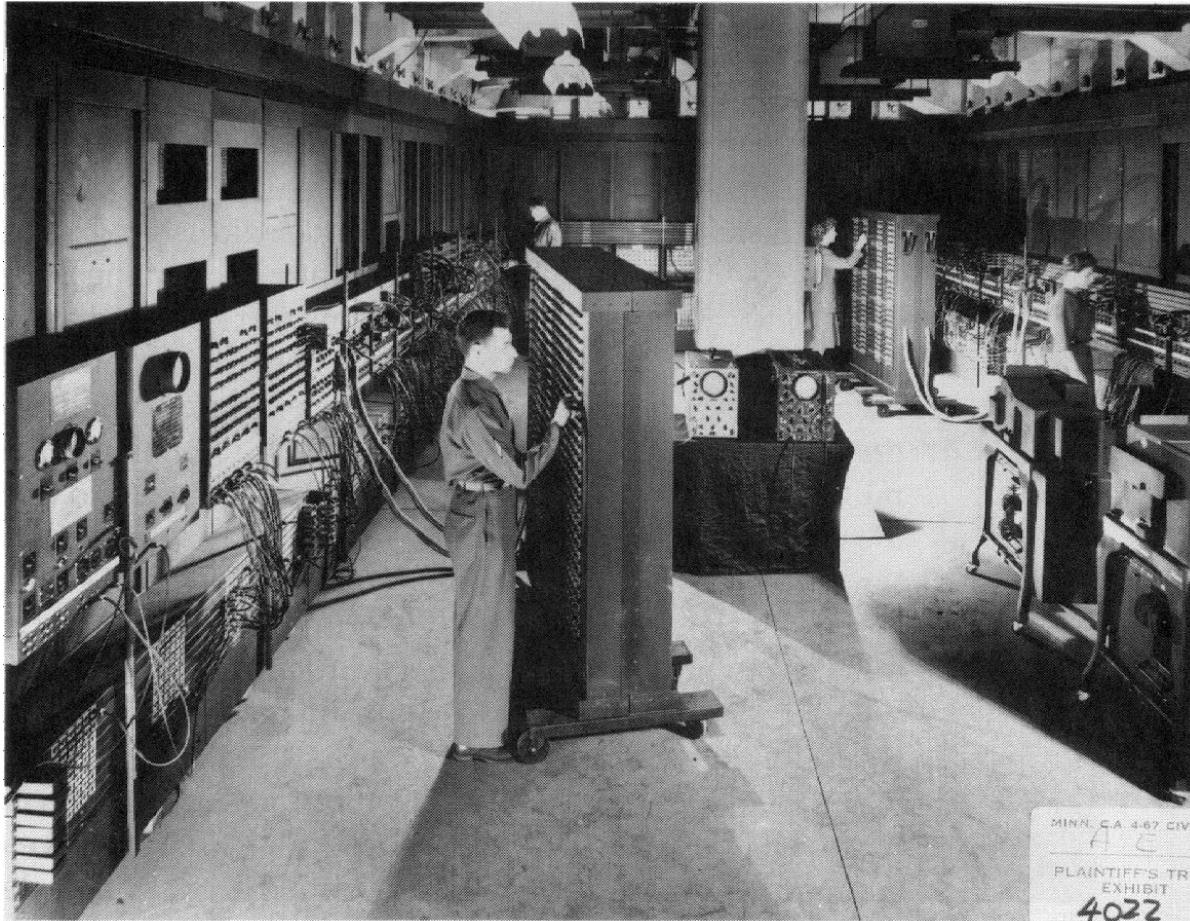


# *First Transistor (Bipolar)*

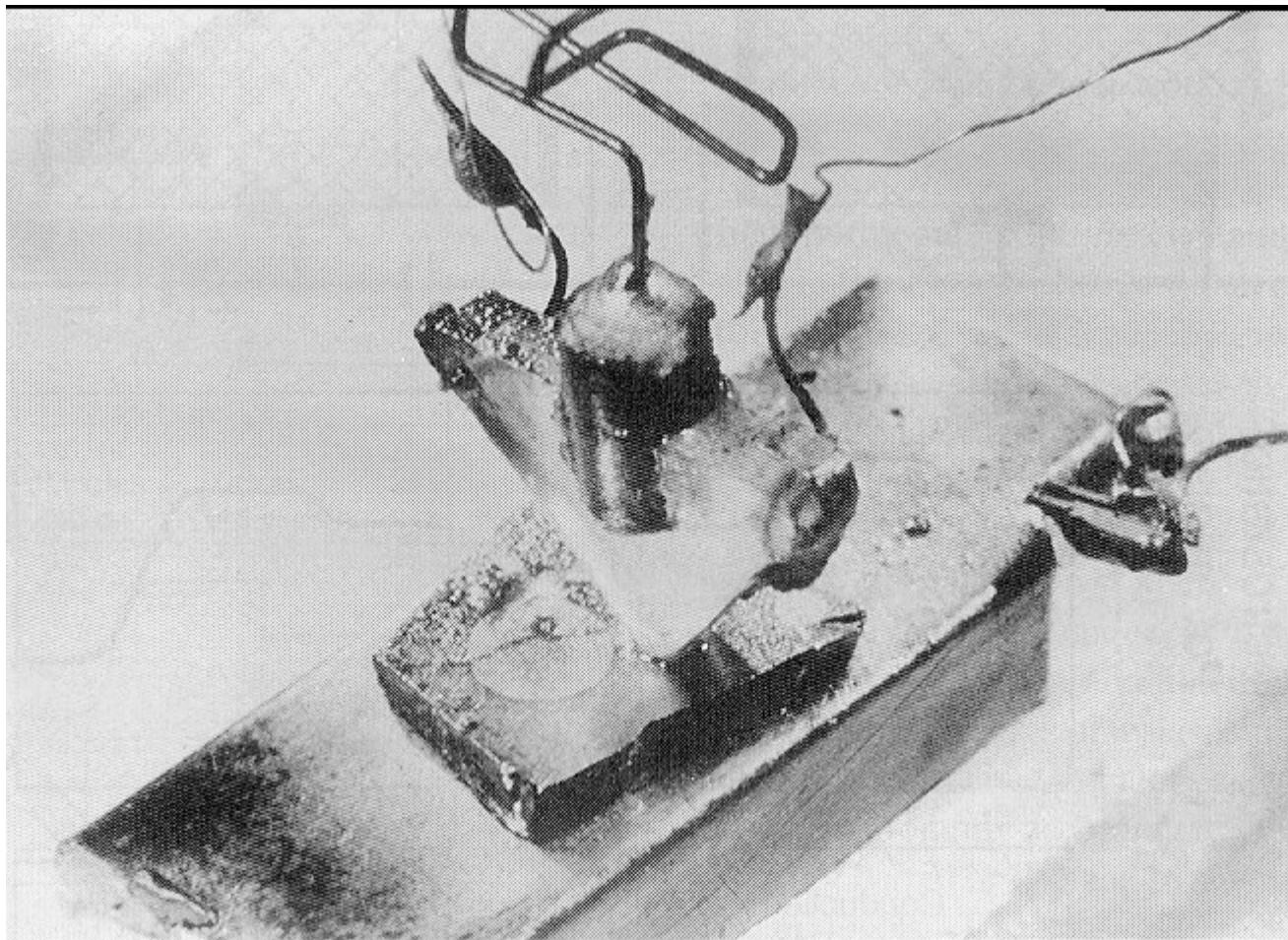

First transistor  
Bell Labs, 1948

# The First Integrated Circuits

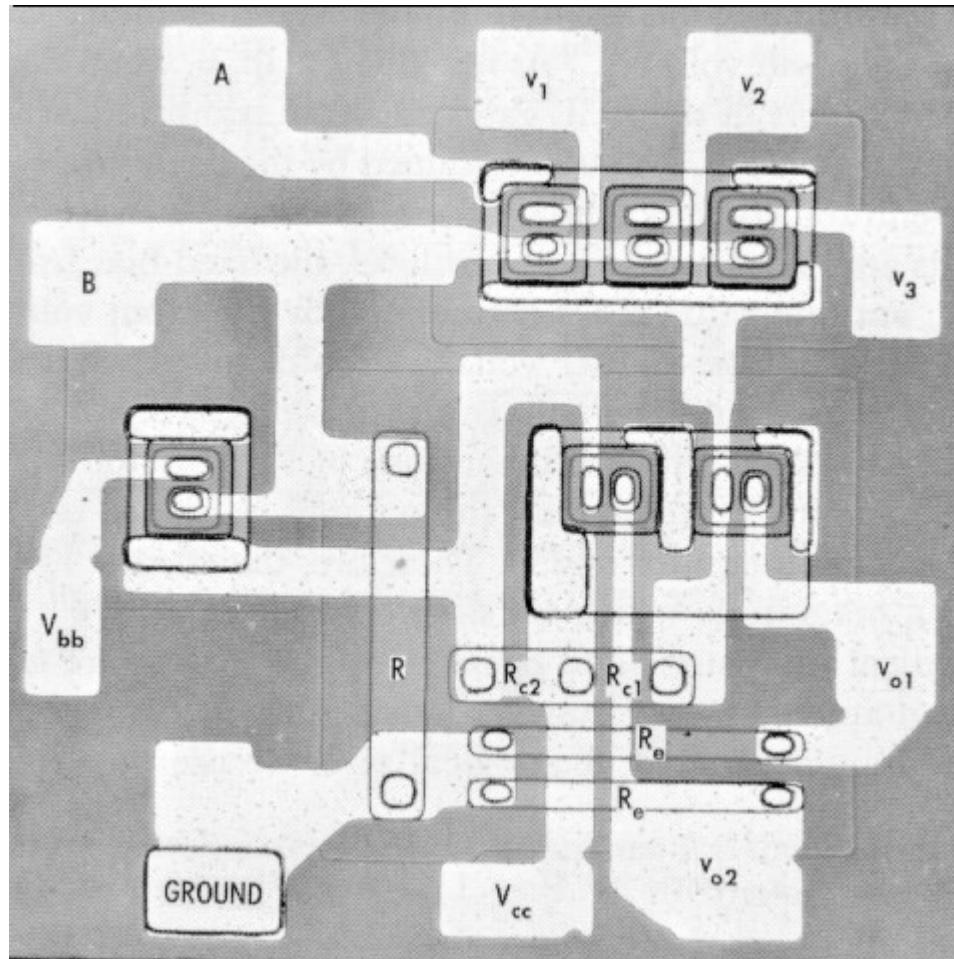


*Bipolar logic  
1960's*


ECL 3-input Gate  
Motorola 1966

# Basic IC circuit component: MOS transistor

MOS: Metal Oxide Semiconductor

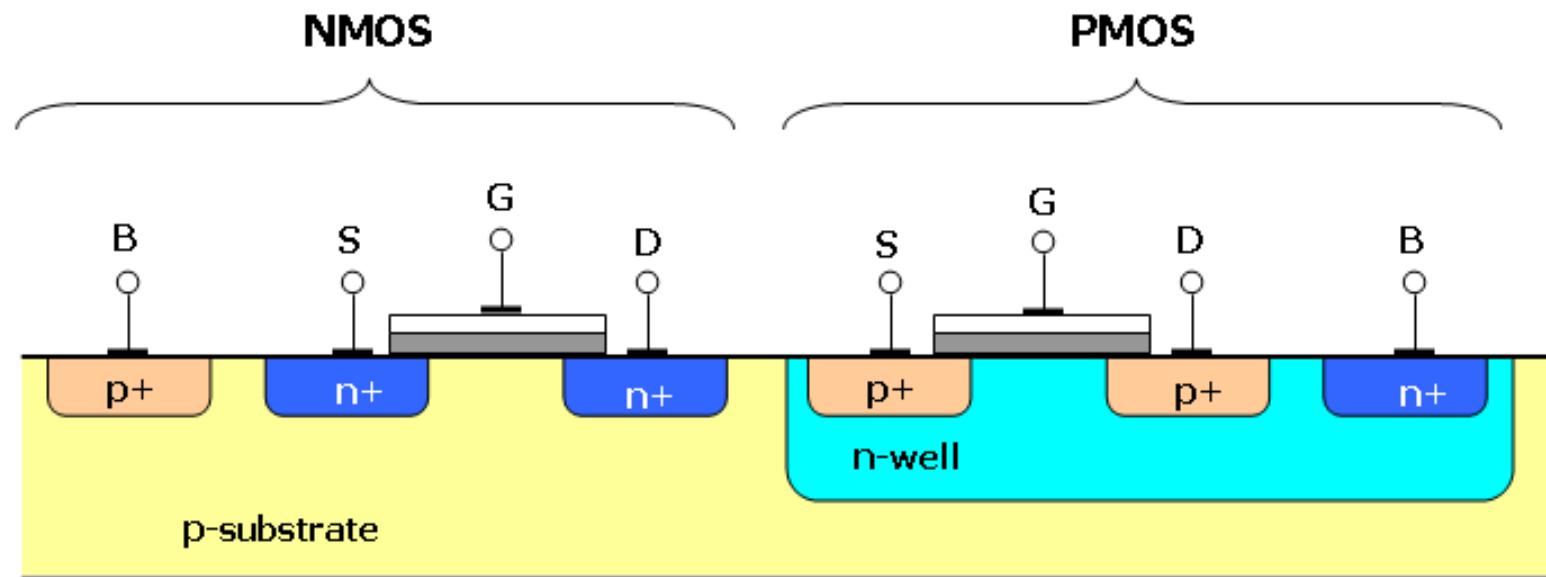


# *Intel 4004 Micro-Processor*

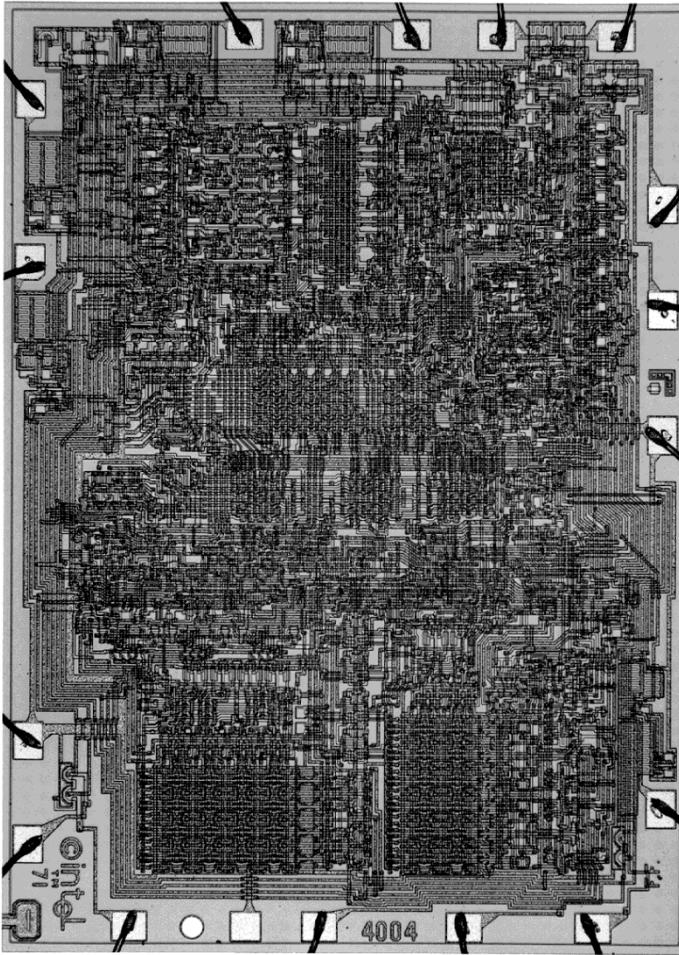


1971  
1000 transistors  
< 1MHz operation  
10 $\mu$ m technology

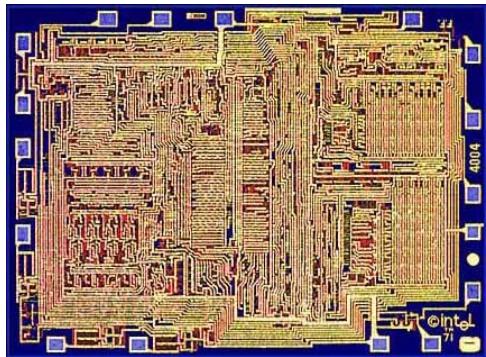
# *Transition to Automation and Regular Structures*




Intel 4004 ('71)

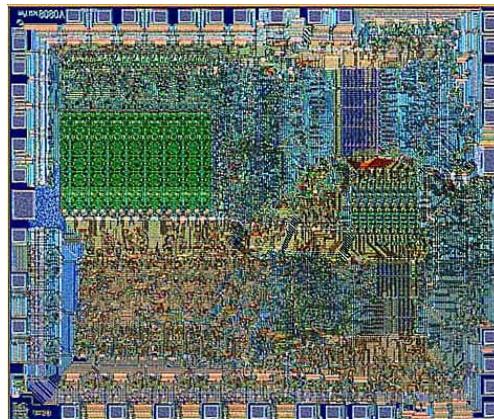


Intel 8080

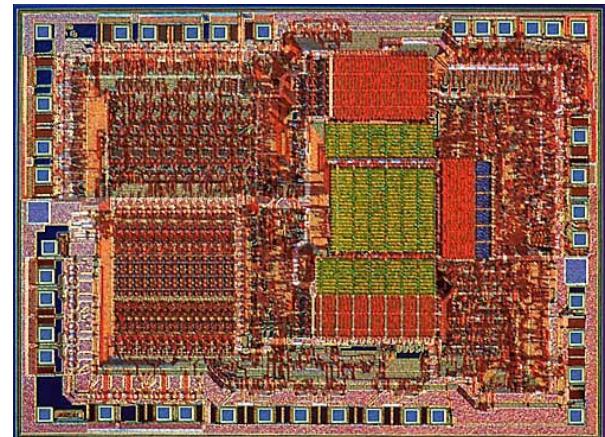

Intel 8085

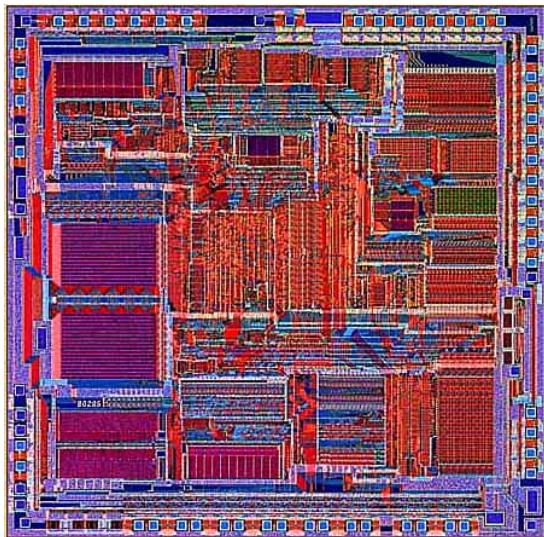


Intel 8286

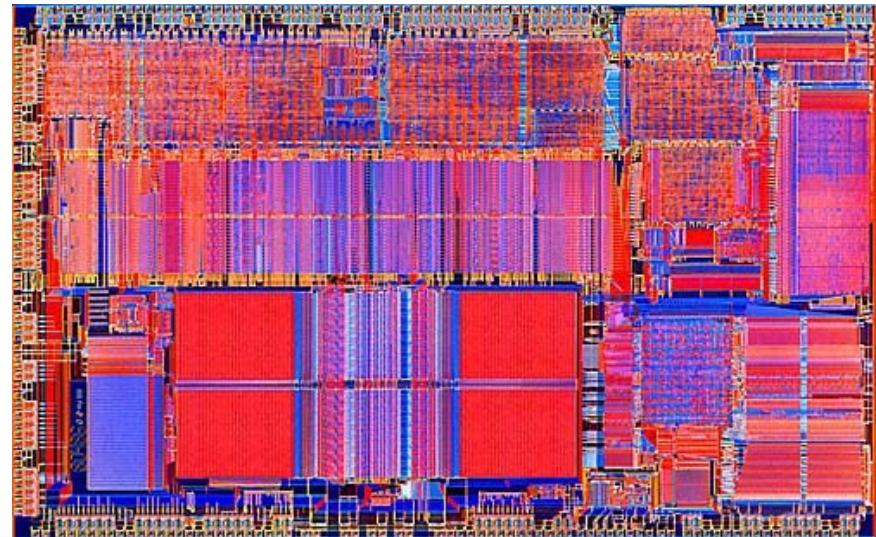

Intel 8486

# *Intel Pentium (IV) microprocessor*

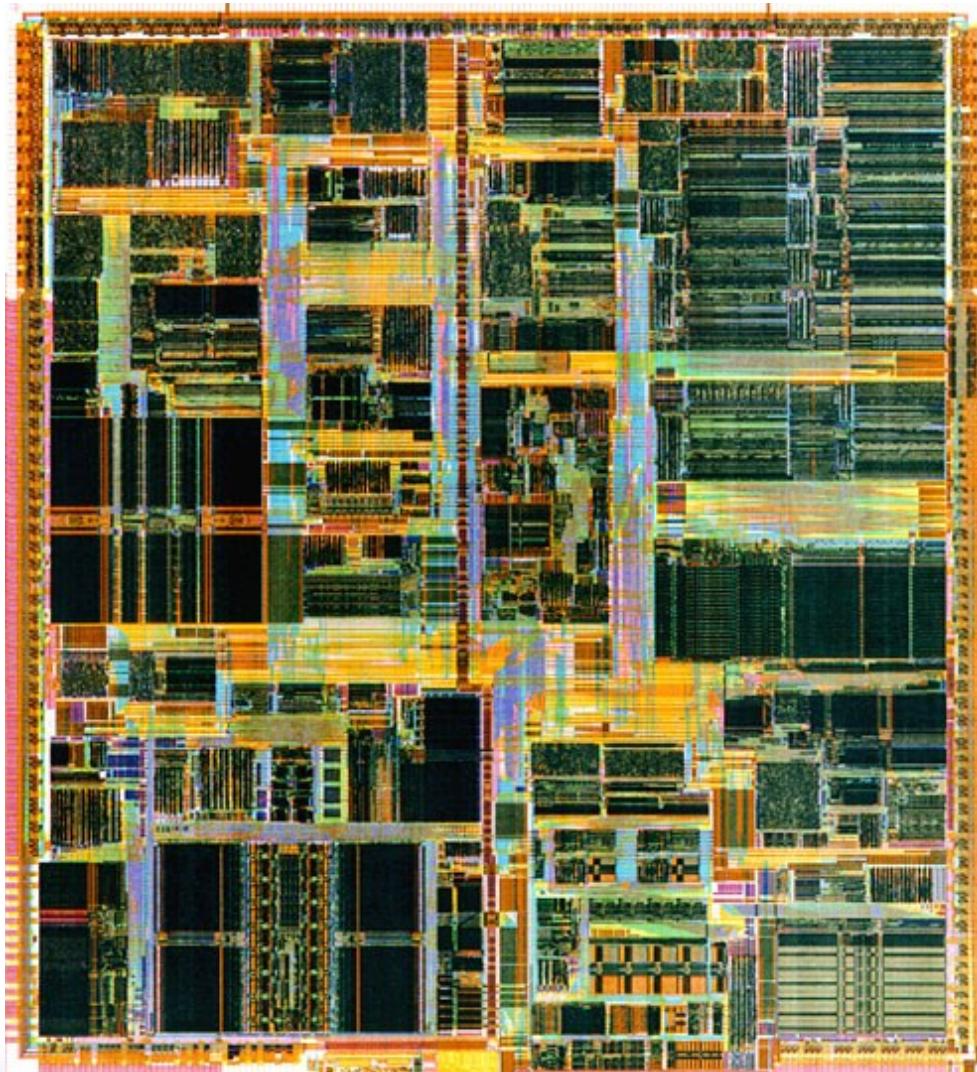

2001

42 Million transistors

1.5 GHz operation

0.18 $\mu$ m technology


# *Intel Core™2 Duo Processor*

2006

291 Million transistors

3 GHz operation

65nm technology

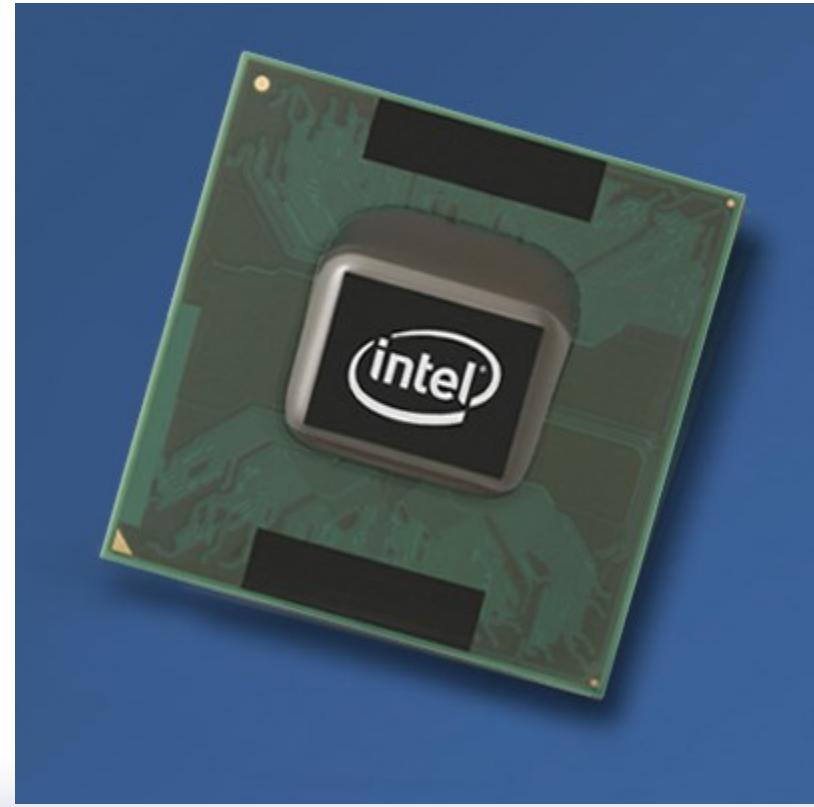

# *More recent Processors*


- 2007
  - 800 Million transistors
  - 2 GHz operation
  - 45nm technology
- 2010 Core i7
  - 1.2 Billion transistors
  - 3.3 GHz operation
  - 32nm technology
- 2012 Core i7 (newer generations)
  - 1.7 Billion transistors
  - 4.0 GHz operation
  - 22nm technology
- 2015 14nm, 2017 10nm, and 2018 7nm, 2019 5nm?

# More recent Processors

Apple A11 Bionic (hexa-core ARM64 "mobile SoC")	4,300,000,000	2017	Apple	10 nm	89 mm <sup>2</sup>
15-core Xeon Ivy Bridge-EX	4,310,000,000 <sup>[36]</sup>	2014	Intel	22 nm	541 mm <sup>2</sup>
8-core Ryzen	4,800,000,000 <sup>[37]</sup>	2017	AMD	14 nm	192 mm <sup>2</sup>
61-core Xeon Phi	5,000,000,000 <sup>[38]</sup>	2012	Intel	22 nm	720 mm <sup>2</sup>
Xbox One main SoC	5,000,000,000	2013	Microsoft/AMD	28 nm	363 mm <sup>2</sup>
18-core Xeon Haswell-E5	5,560,000,000 <sup>[39]</sup>	2014	Intel	22 nm	661 mm <sup>2</sup>
IBM z14	6,100,000,000	2017	IBM	14 nm	696 mm <sup>2</sup>
Xbox One X (Project Scorpio) main SoC	7,000,000,000 <sup>[40]</sup>	2017	Microsoft/AMD	16 nm	360 mm <sup>2</sup> <sup>[40]</sup>
IBM z13 Storage Controller	7,100,000,000	2015	IBM	22 nm	678 mm <sup>2</sup>
22-core Xeon Broadwell-E5	7,200,000,000 <sup>[41]</sup>	2016	Intel	14 nm	456 mm <sup>2</sup>
POWER9	8,000,000,000	2017	IBM	14 nm	695 mm <sup>2</sup>
72-core Xeon Phi	8,000,000,000	2016	Intel	14 nm	683 mm <sup>2</sup>
IBM z14 Storage Controller	9,700,000,000	2017	IBM	14 nm	696 mm <sup>2</sup>
32-core SPARC M7	10,000,000,000 <sup>[42]</sup>	2015	Oracle	20 nm	
Centriq 2400	18,000,000,000 <sup>[43]</sup>	2017	Qualcomm	10 nm	398 mm <sup>2</sup>
32-core AMD Epyc	19,200,000,000	2017	AMD	14 nm	768 mm <sup>2</sup> (4 x 192 mm <sup>2</sup> )


Source: [https://en.wikipedia.org/wiki/Transistor\\_count](https://en.wikipedia.org/wiki/Transistor_count)

# Power Consumption

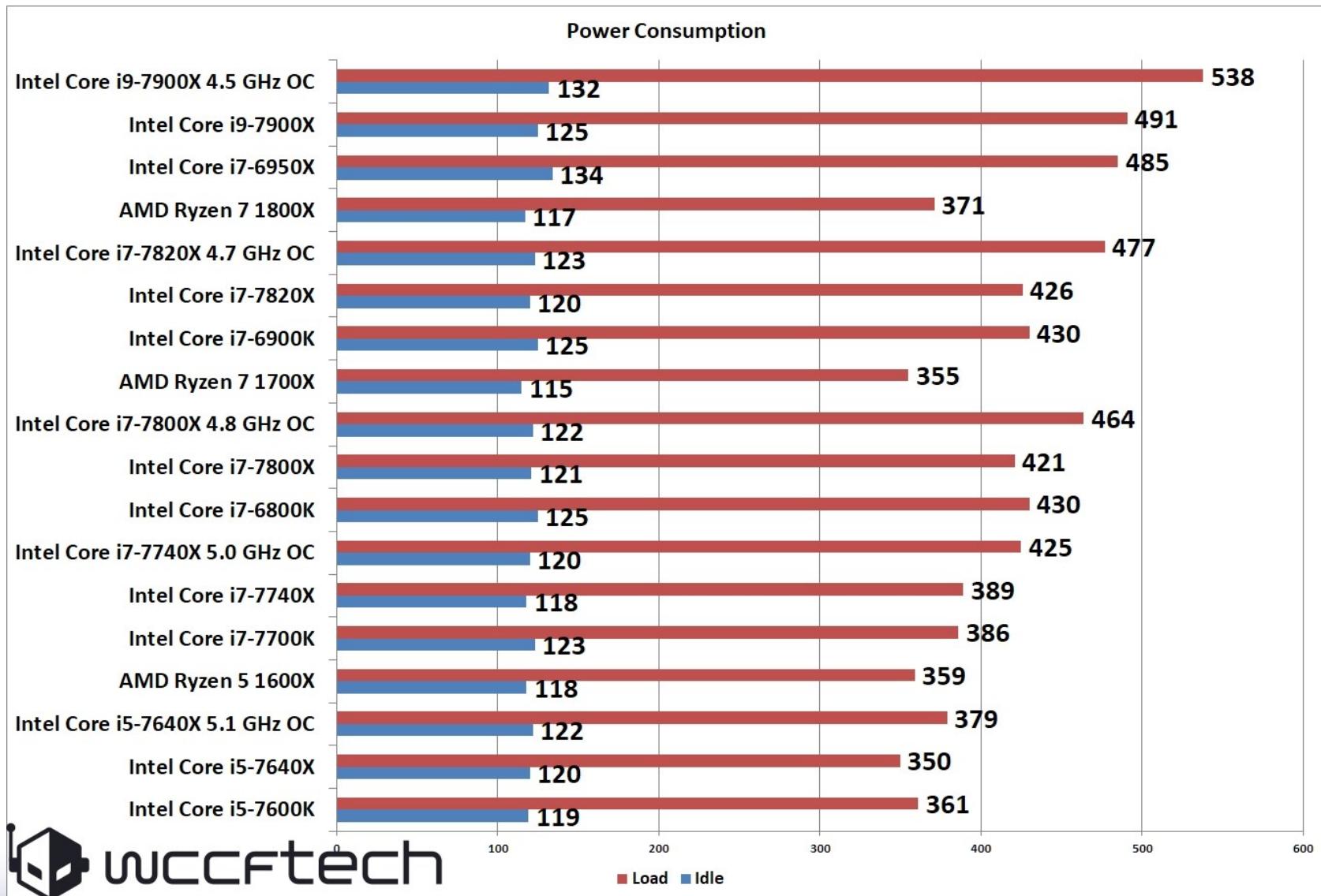

# Power density

*Thermal hot spots*

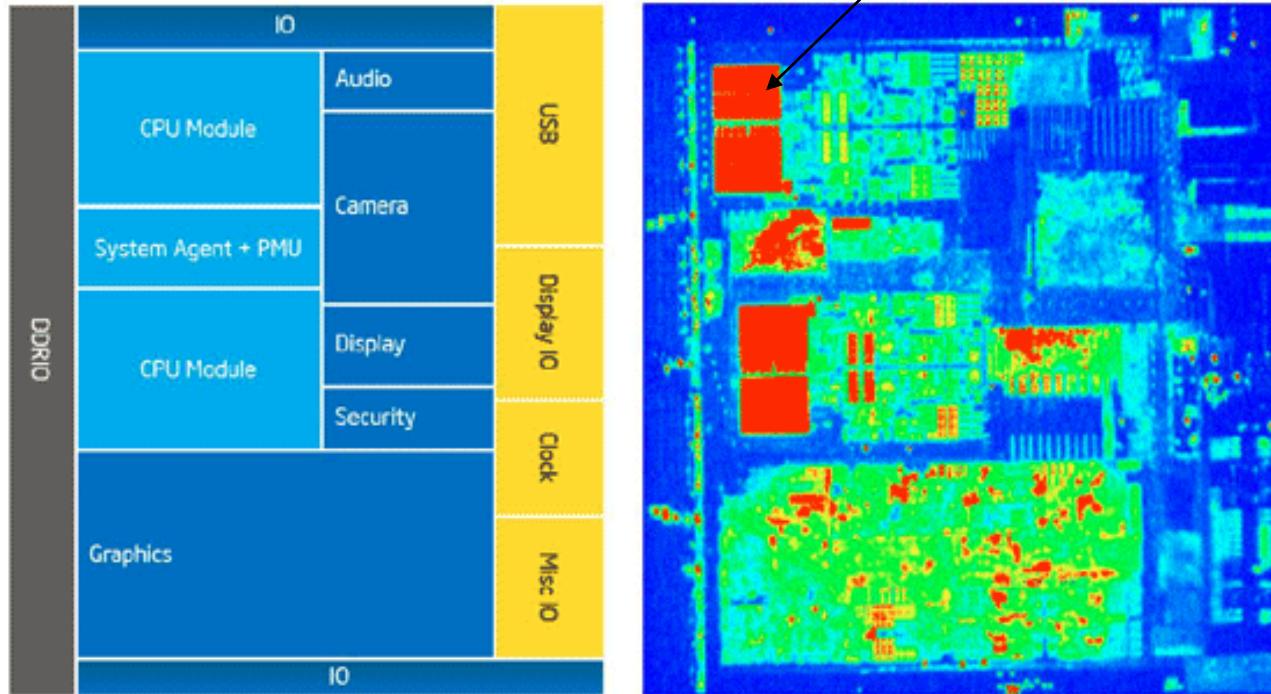

1. Hot spots are smaller in relation to the total die size
2. Scaling typically do NOT reduce power more than they reduce size (say from 90 nm → 14 nm)
3. multi-core? Lowpower technologies?

Source: <https://forums.anandtech.com/threads/cpu-power-density-trend.2416388/>


# *Not Only Microprocessors*

Cell Phone


HDTV

PDA

....

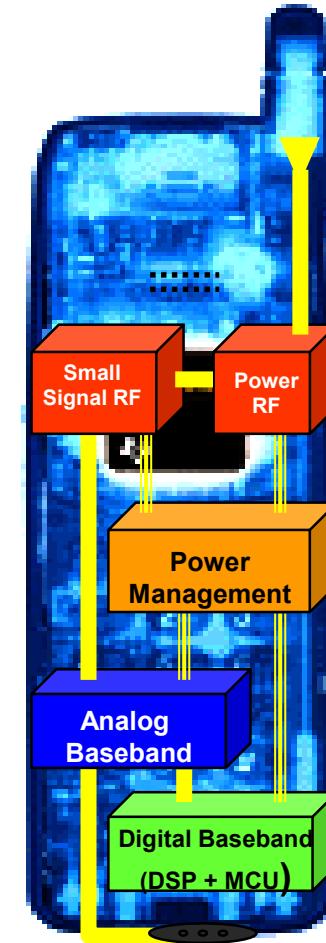

# Booming Mobile and IoT Applications


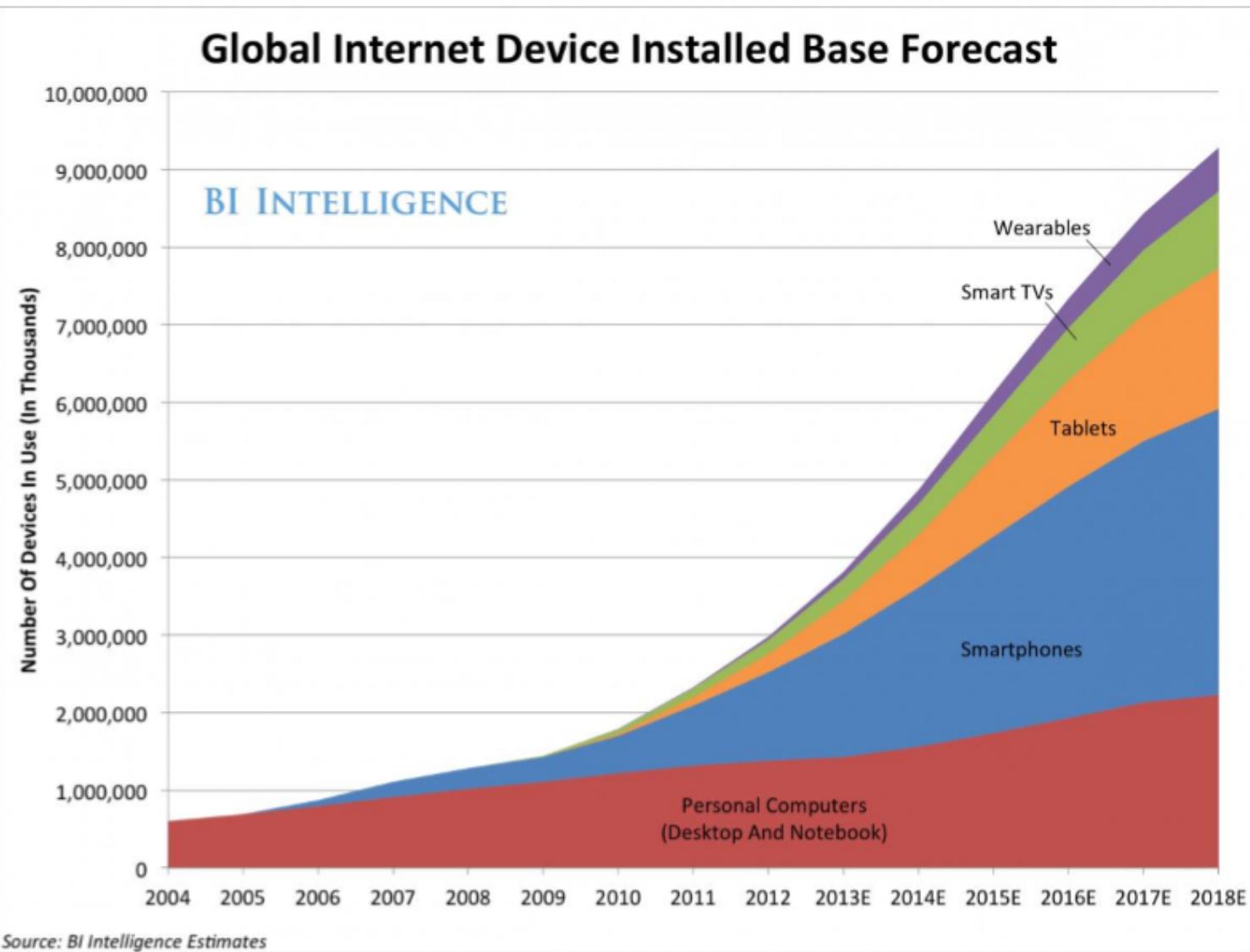


# *What is a MOS Transistor?*


A Switch!



An MOS Transistor

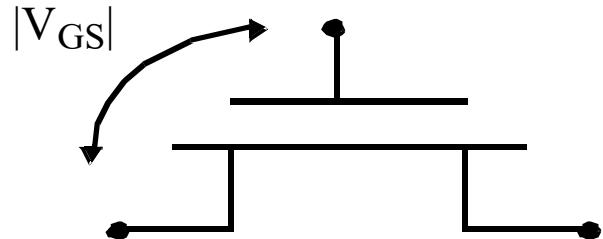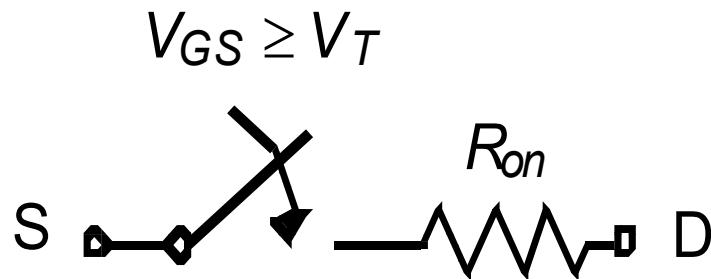


# *MOS Transistors - Types and Symbols*

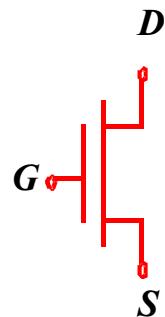

if  $G=“1”$  or Vdd  
switch on


**NMOS**

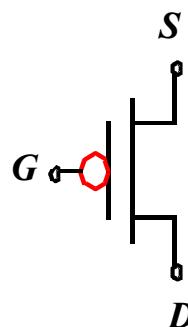

if  $G=“0”$  or Gnd  
switch on


**PMOS**

# The CMOS Inverter: A First Glance

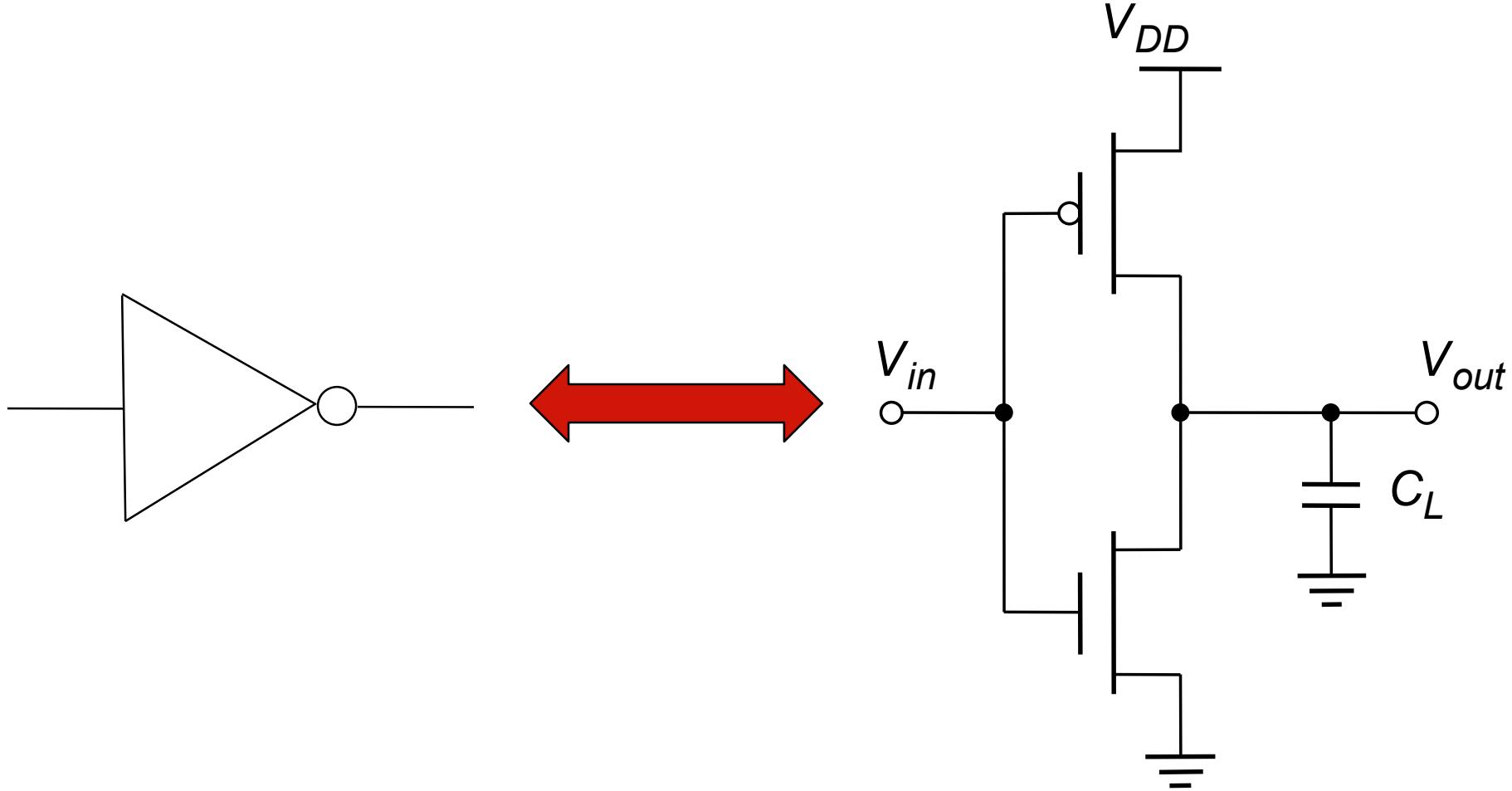


# *CMOS Inverter*

## *First-Order DC Analysis*

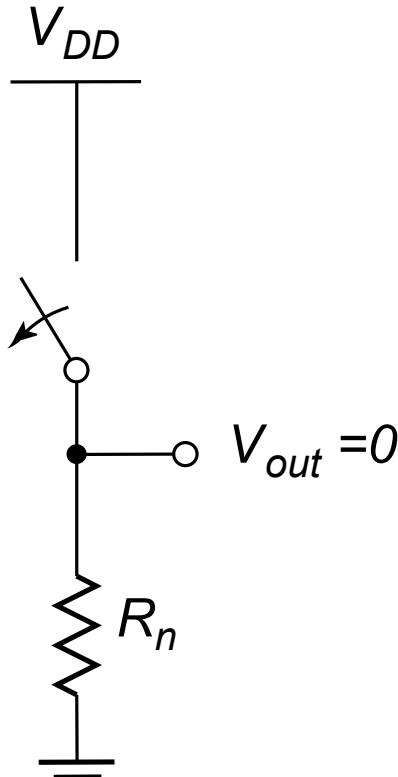

$$V_{in} = V_{DD}$$

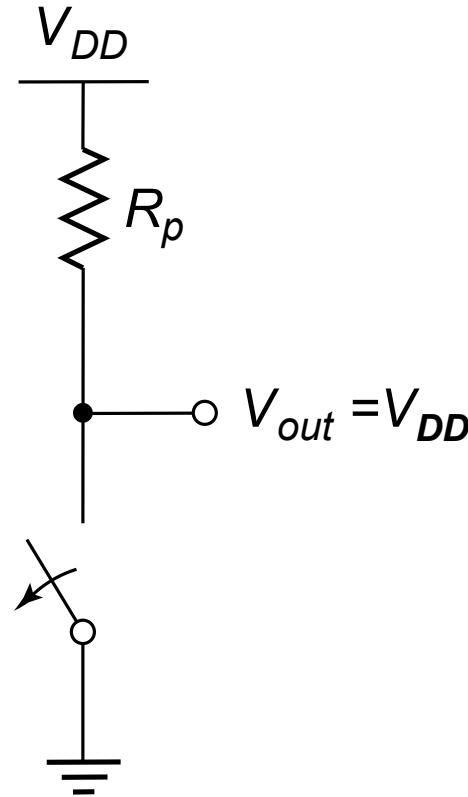


$$V_{in} = 0$$
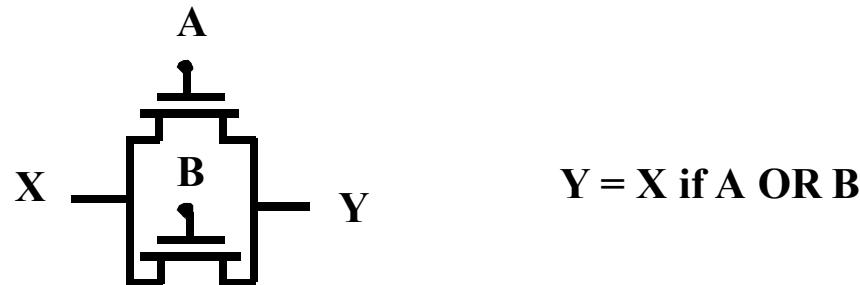
# NMOS Transistors in Series/Parallel Connection

Transistors can be thought as a switch controlled by its gate signal



NMOS switch closes when switch control input is high



NMOS Transistors pass a “strong” 0 but a “weak” 1
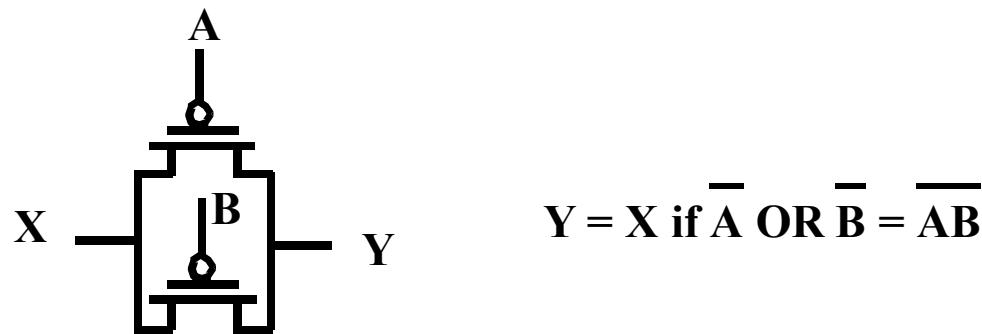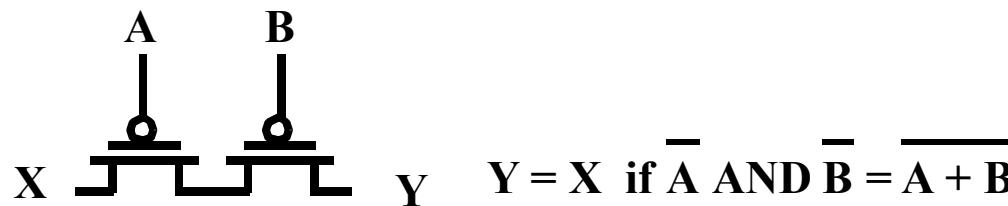
# PMOS Transistors in Series/Parallel Connection

PMOS switch closes when switch control input is low




PMOS Transistors pass a “strong” 1 but a “weak” 0

# Example Gate: NAND

A	B	Out
0	0	1
0	1	1
1	0	1
1	1	0

Truth Table of a 2 input NAND gate

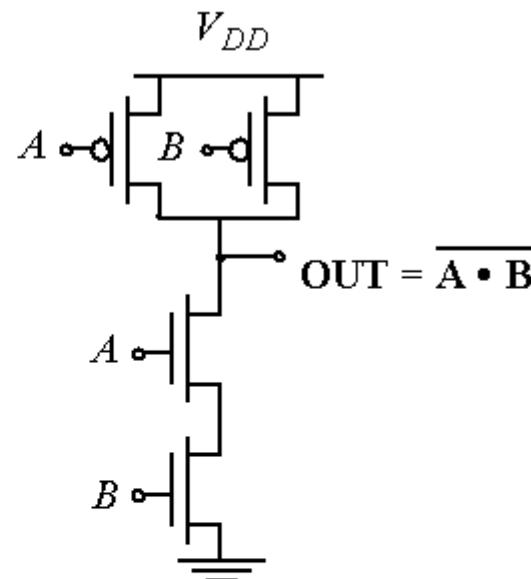

PDN:  $G = A \cdot B \Rightarrow$  Conduction to GND


PUN:  $F = \overline{\overline{A} + \overline{B}} = \overline{AB} \Rightarrow$  Conduction to V<sub>DD</sub>

$$\overline{G(\overline{In_1}, \overline{In_2}, \overline{In_3}, \dots)} \equiv F(\overline{In_1}, \overline{In_2}, \overline{In_3}, \dots)$$


# Example Gate: NOR

A	B	Out
0	0	1
0	1	0
1	0	0
1	1	0

Truth Table of a 2 input NOR gate

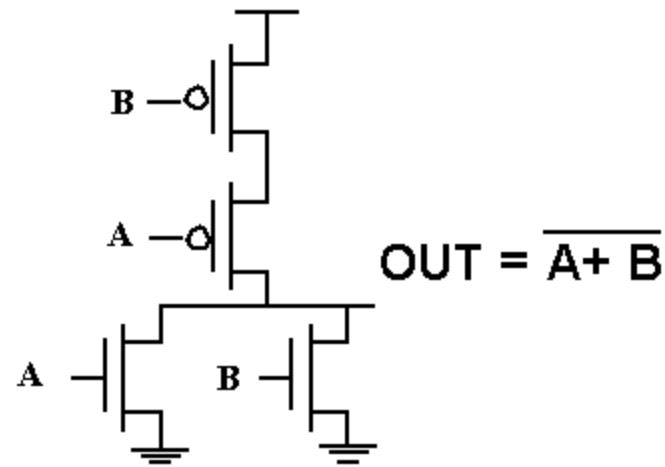


# Full-Adder

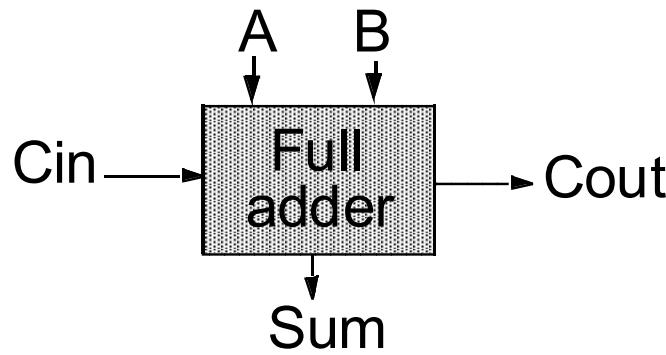

$A$	$B$	$C_i$	$S$	$C_o$
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


# The Binary Adder

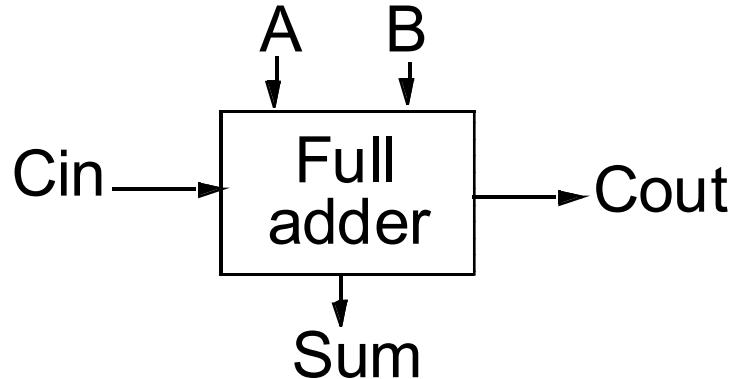

$$\begin{aligned} S &= A \oplus B \oplus C_i \\ &= A\bar{B}\bar{C}_i + \bar{A}B\bar{C}_i + \bar{A}\bar{B}C_i + ABC_i \end{aligned}$$


$$C_o = AB + BC_i + AC_i$$

# Complimentary Static CMOS Full Adder

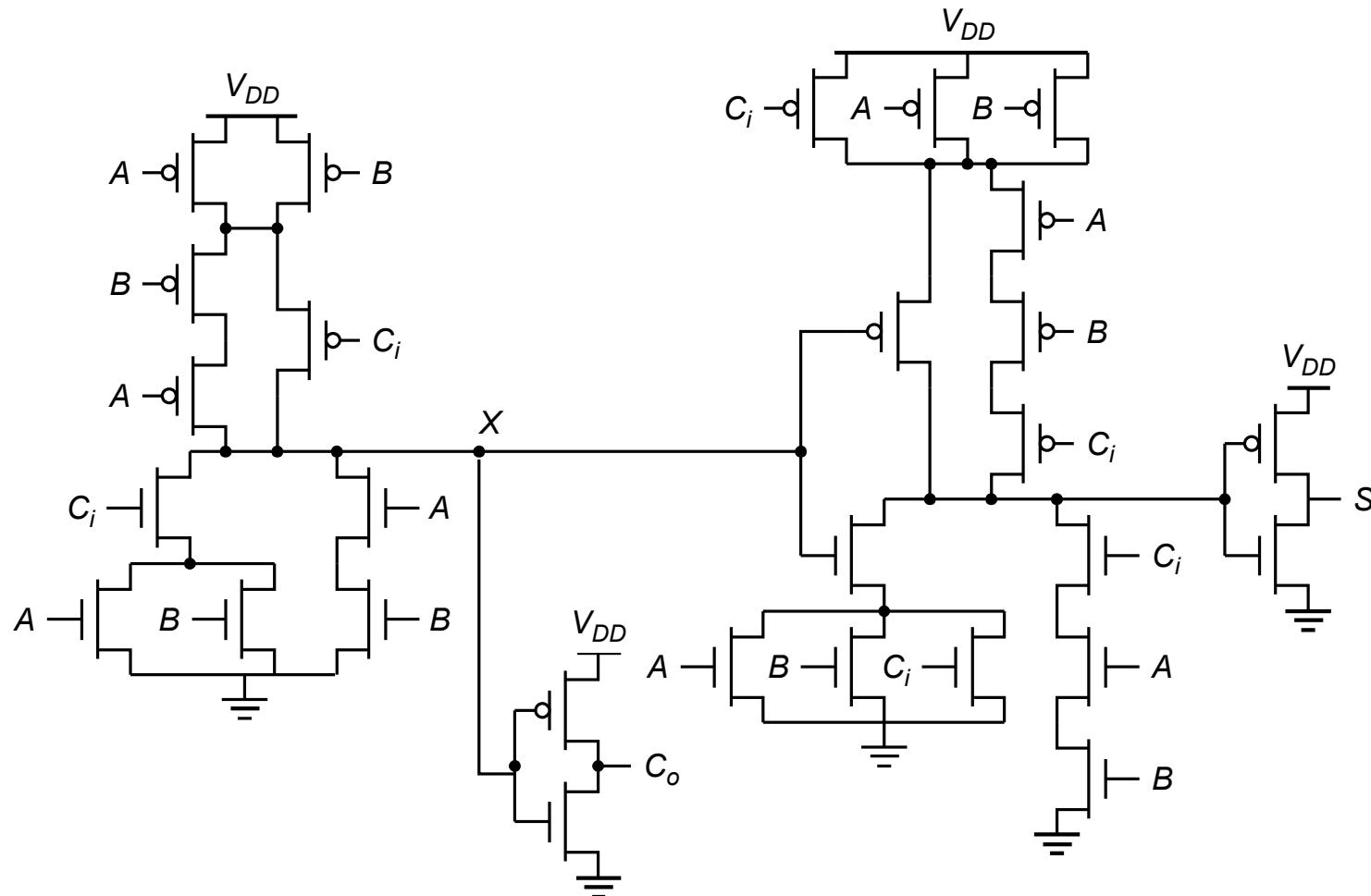


28 Transistors

# The Ripple-Carry Adder

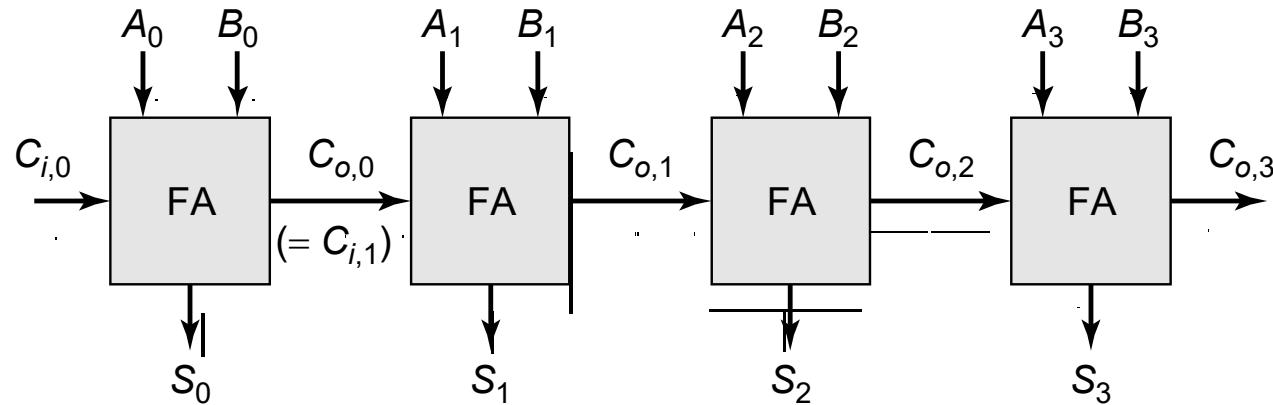

# *SRAM Memory cell*

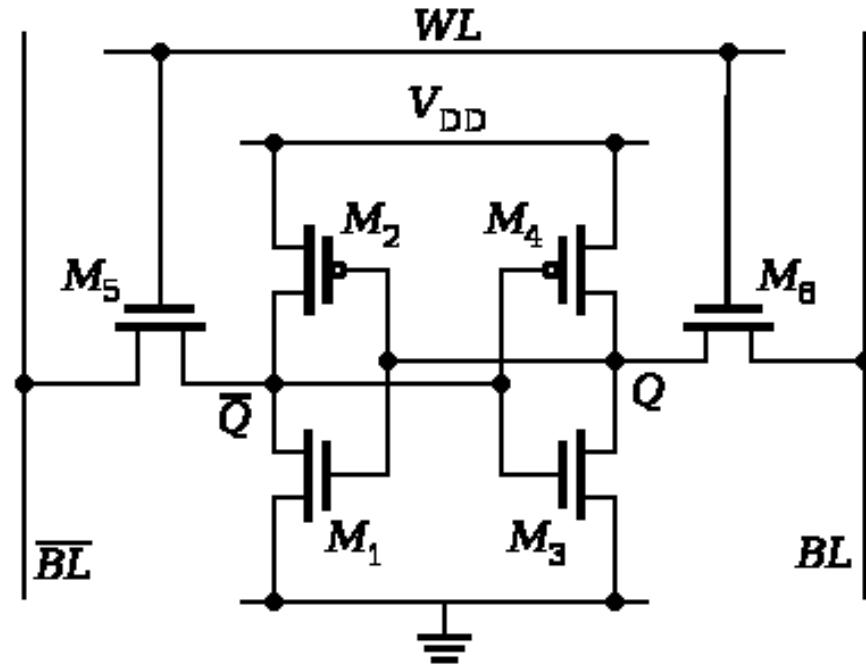


# *The add-up*


32-bit adder:	>3,000
32-bit comparator:	>3,000
32-bit multiplier:	>50,000
1k SRAM:	6,000

...

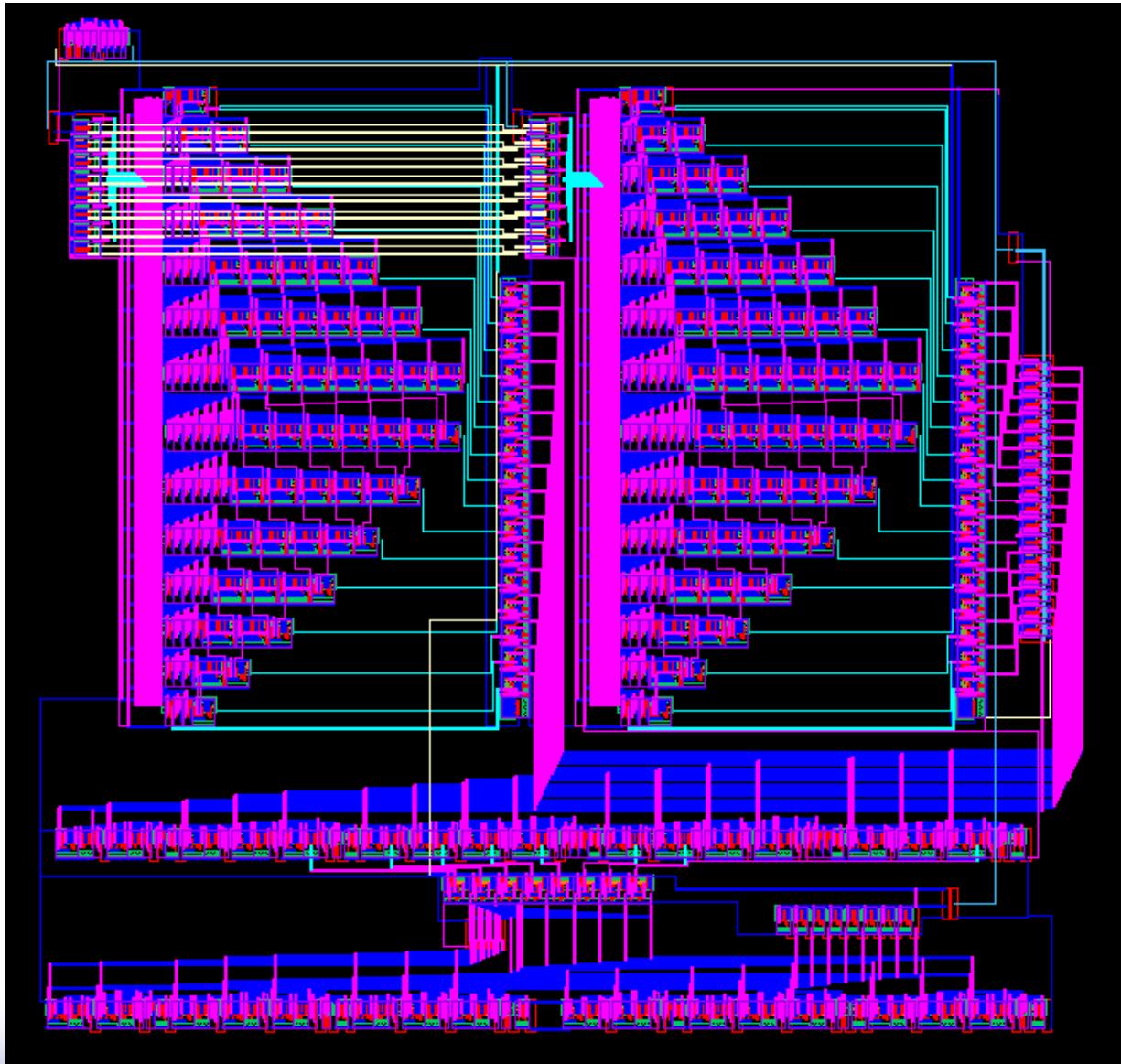
# *Example project: FFT Butterfly Unit Layout*



# 8-bit CPU Layout

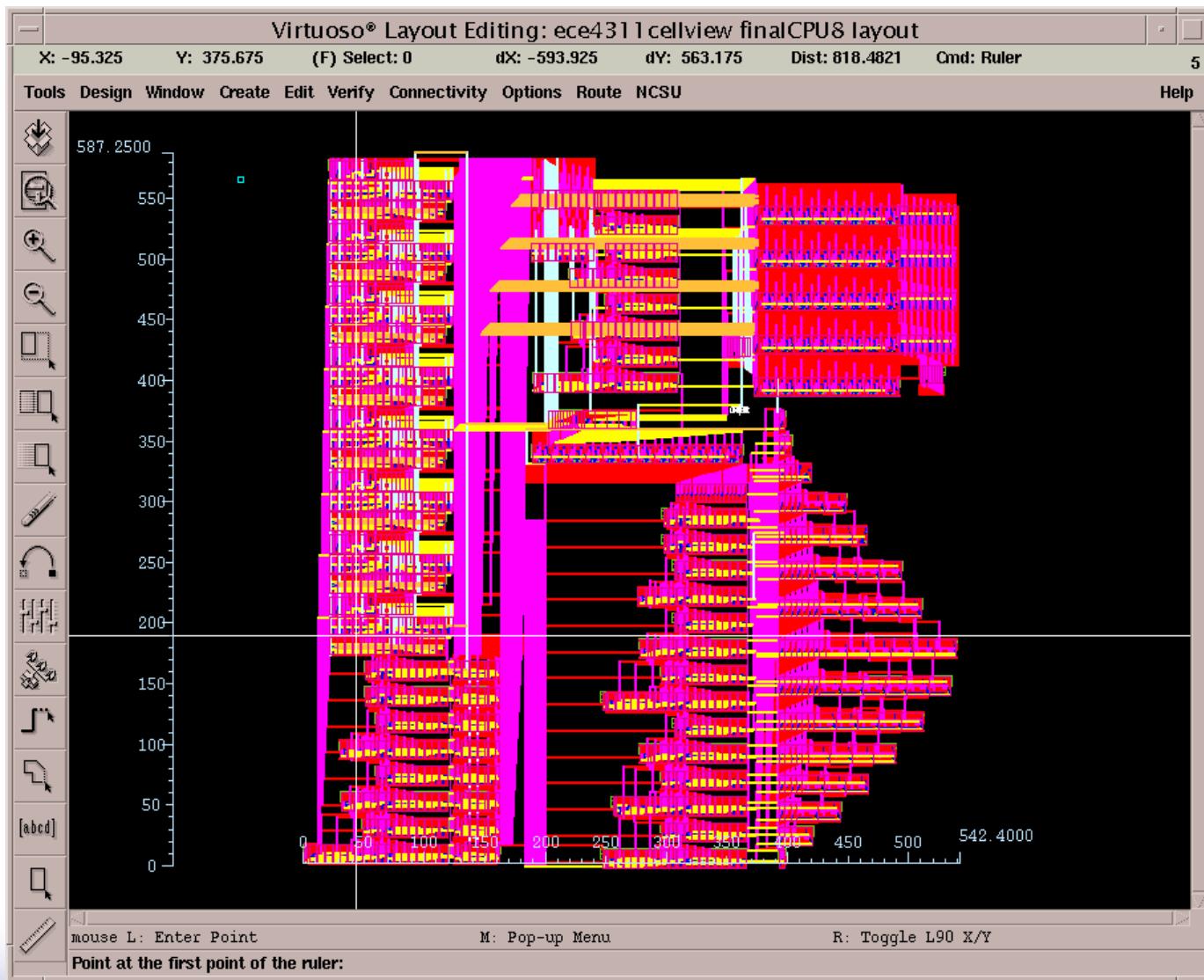

# *FIR Filter*

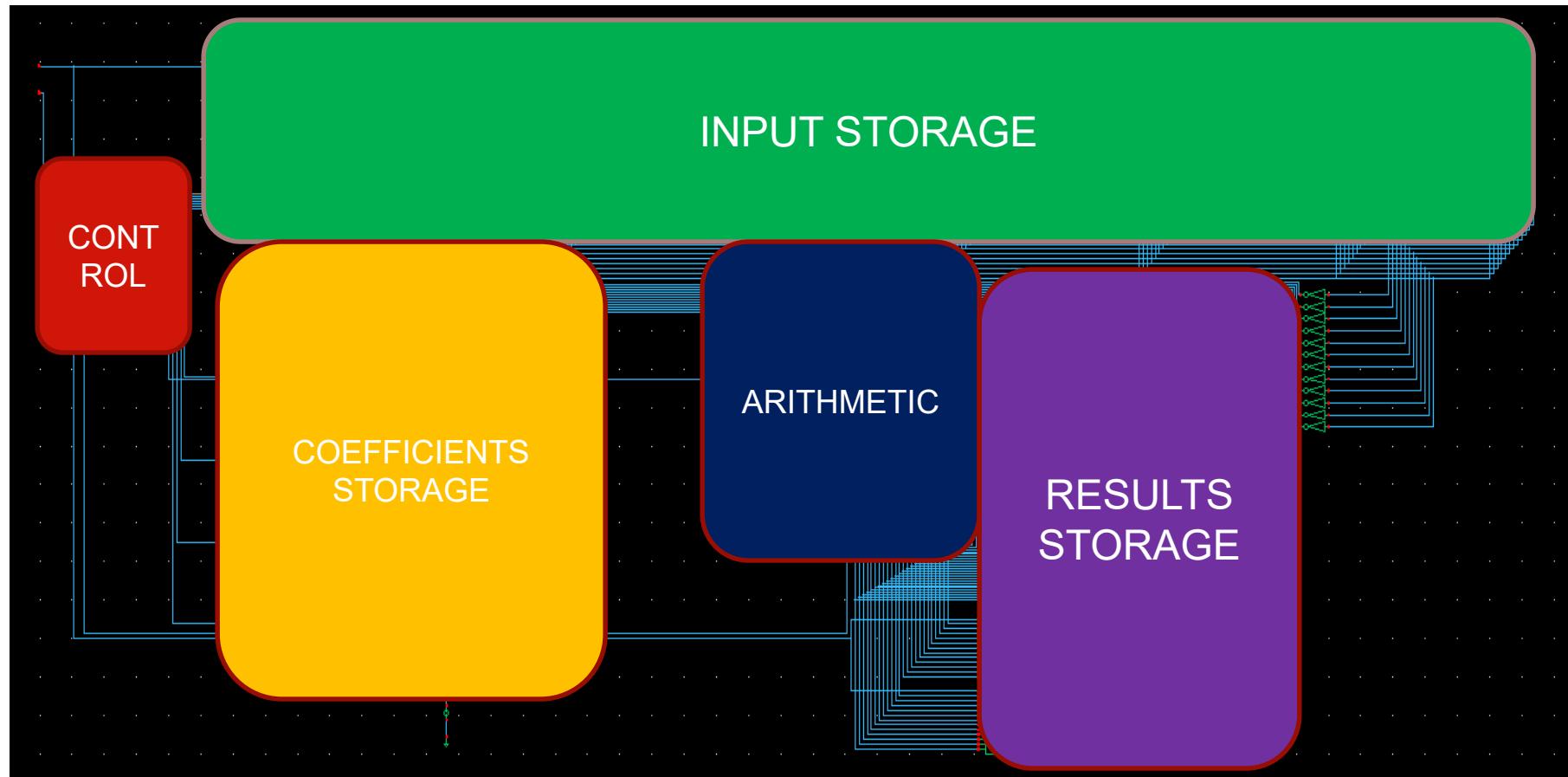

**Module 1 – Control Module**



**Module 2 – Input Module**

**Module 3 – Coefficients Module**

**Module 4 – Arithmetic Module**

**Module 5 – Results Storage**

# A Delta-Sigma A/C Converter

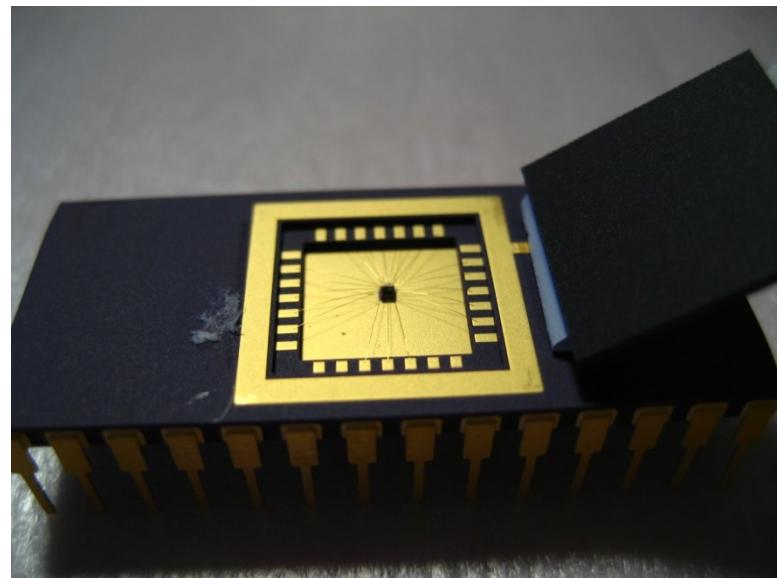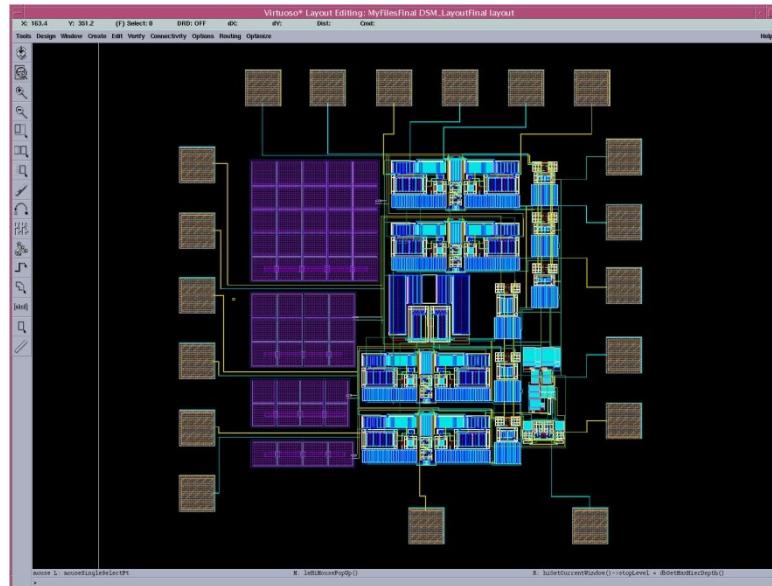


By: Matt Webb, Hairong Chang  
Introduction

# Career in VLSI/IC



- Intel, AMD, Texas Ins.,,...
- National Semi., Cypress Semi,....
- Apple, Qualcomm, Broadcom, Samsung,....
- Micron, Seagate, WesternDigital...
- Cadence, Synopsys, MentorGraphics...
- Xilinx, Altera, ....
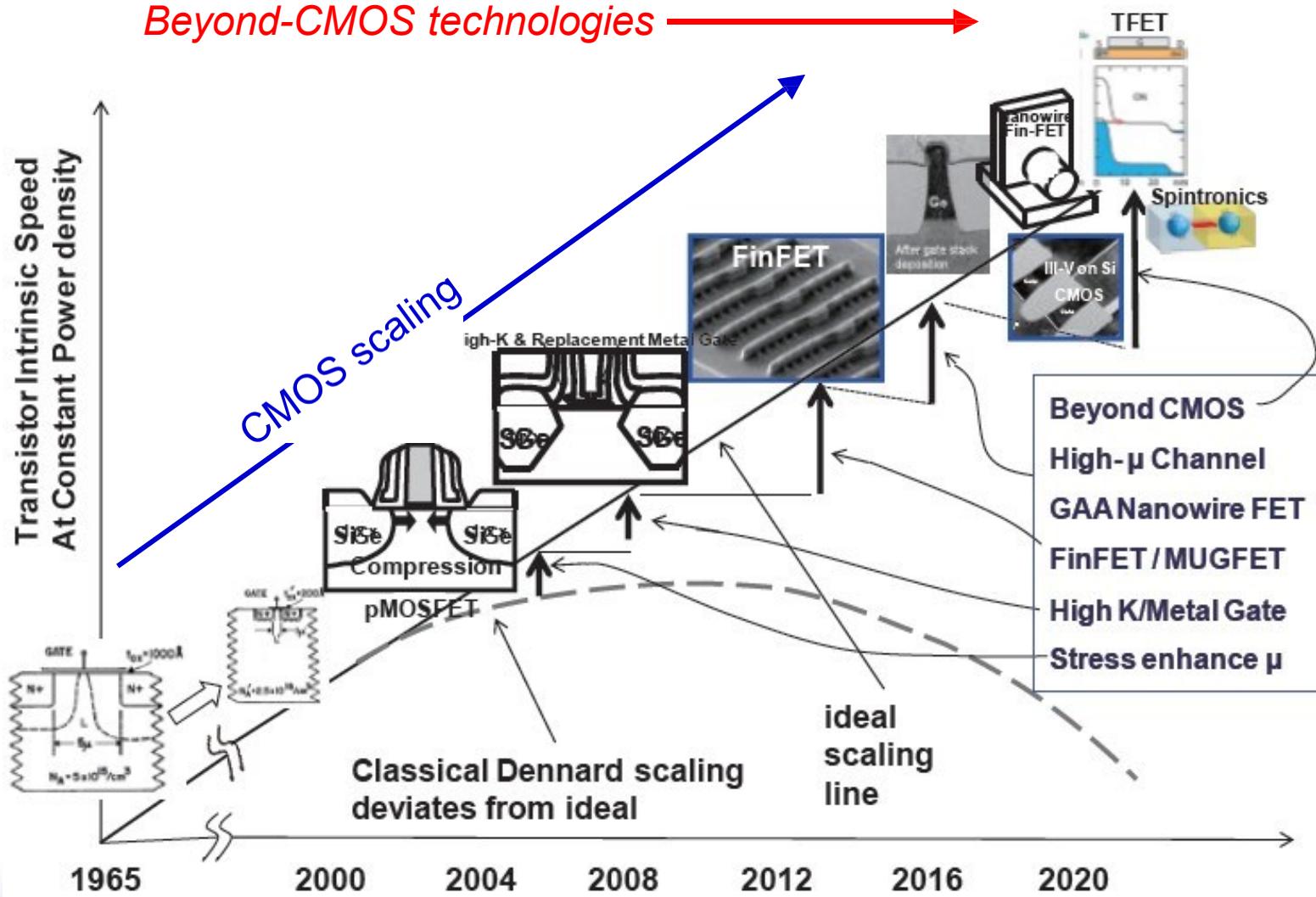
# Technology Innovations Driven by Scaling



# Contact Information:

Office: MWAH 276

Hour: 10-11am, MTWF

Phone: 726-7095

Email: [htang@d.umn.edu](mailto:htang@d.umn.edu)

Http: [www.d.umn.edu/~htang](http://www.d.umn.edu/~htang)